

## Binary Logics:

→ Consist of binary variables and logical operation

- $A, B, C, x, y, z$
- possible values  $[0, 1]$
- AND
- OR
- NOT
- etc.

## Logic Gates:

- Most Basic Digital Device
- 1 or more input & 1 outputs
- Output follows a certain logics

## Truthtable:

→ A list of all possible inputs and outputs

## All logic gates


NOT, AND, OR, XOR  
NAND, NOR, XNOR

\* NOT, AND, OR are Basic gates.

\* NAND & NOR are universal gate.

A universal gate is a gate which can implement any other gate.


AND:

 

\* Output 1 when all inputs are 1.

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1


OR:

 

\* Output 1 when atleast one input is 1

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1


NOT (Inverter)

 


A	A'
0	1
1	0

\* Output is inverse of input

NAND

 


aka

 


A	B	(AB)'
0	0	1
0	1	1
1	0	1
1	1	0

\* Inverse of AND

NOR

 


aka

 

A	B	(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

\* Inverse of OR


## XOR

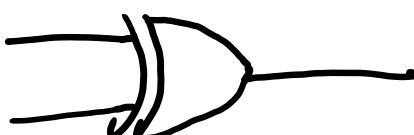$A$   
 $B$    $A \oplus B = AB' + A'B$

Output 1 if odd number of input is 1

A	B	$(A \oplus B)'$
0	0	0
0	1	1
1	0	1
1	1	0


## XNOR :

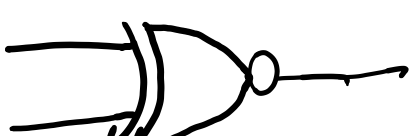$A$   
 $B$    $A \odot B = AB + A'B$


A	B	$(A \odot B)'$
0	0	1
0	1	0
1	0	0
1	1	1


Inverse of XOR

## Basic Gates using NAND :

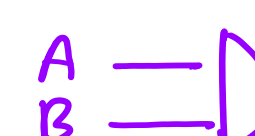
NAND  $A$   
 $B$    $(AB)'$


NOT

$A$    $A'$

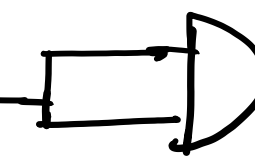
$A$    $(AA)' = A'$


AND

$A$   
 $B$    $AB$

$A$   
 $B$    $((AB)')' = AB$

OR

$A$   
 $B$    $A+B$

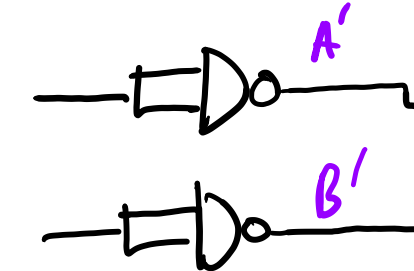$A$    $(A'B')'$   
 $B$   $= (A')' + (B')'$   
 $= A+B$

→ Using DeMorgan's law

## Basic Gates using NOR :

NOR  $A \quad B \Rightarrow \neg(A+B)$

NOT  $A \Rightarrow A'$

OR  $A \quad B \Rightarrow A+B$

AND  $A \quad B \Rightarrow AB$

$A \Rightarrow (A+A)' = A'$

$A \quad B \Rightarrow (A+B)' \Rightarrow ((A+B)')' = A+B$

$A \quad B \Rightarrow (A'+B')' = (A')' \cdot (B')' = AB$   
 Demorgan's law

## Proof using Truth table:


\* Proof that  $\underbrace{x \cdot (y+z)}_{LHS} = \underbrace{(x \cdot y) + (x \cdot z)}_{RHS}$

<u>x</u>	<u>y</u>	<u>z</u>	<u>y+z</u>	<u><math>x \cdot (y+z)</math></u>	<u><math>x \cdot y</math></u>	<u><math>x \cdot z</math></u>	<u><math>(x \cdot y) + (x \cdot z)</math></u>
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

∴ LHS = RHS.

Implement  $(AB)c' + (A' + B' + cA')$  using Basic Gates

A B C

 

# Boolean Algebra

## Basic theorem of Boolean Algebra

\* Theorem can be proved using Truth table or Algebraic Manipulation

Basic Theorems are:

$\Rightarrow x + 0 = x$	$x \cdot 0 = x$	Identity
$\Rightarrow x + x' = 1$	$x \cdot x' = 0$	
$\Rightarrow x + x = x$	$x \cdot x = x$	complement
$\Rightarrow x + 1 = 1$	$x \cdot 0 = 0$	
$\Rightarrow (x')' = x$		
$\Rightarrow x + y = y + x$	$x \cdot y = y \cdot x$	
$\Rightarrow x(yz) = (xy)z$	$x + (y + z) = (x + y) + z$	commutative
* $\Rightarrow x(y + z) = xy + xz$	* $x + yz = (x + y)(x + z)$	
* $\Rightarrow (x + y)' = x'y'$	* $(xy)' = x' + y'$	Distributive
* $\Rightarrow x + xy = x$	* $x(x + y) = x$	
		De Morgan
		Absorption

\* All are important but student tend to forget star marked ones while simplifying

## Duality Principle :

\* If we interchange operators and elements as follows,

$$(OR) + \rightleftharpoons \cdot (AND)$$

$$0 \rightleftharpoons 1$$

Example:

$$\text{if } \underline{a} + (\underline{b} \cdot \underline{c}) + \underline{0} = (\underline{a} + \underline{b}) \cdot (\underline{a} + \underline{c}) \cdot \underline{1}$$

then we can find its dual expression

$$\underline{a} \cdot (\underline{b} + \underline{c}) \cdot \underline{1} = (\underline{a} \cdot \underline{b}) + (\underline{b} \cdot \underline{c}) + \underline{0}$$

\* Duality Gives us free theorems

If a theorem/expression for example,

$$x + 1 = 1 \quad \text{is valid / Proved.}$$

then its dual expression,

$$x \cdot 0 = 0 \quad \text{is also valid / proved}$$



## Operator Precedence:

Parentesis  $\longrightarrow$  NOT  $\longrightarrow$  AND  $\longrightarrow$  OR  
Highest Lowest

## Boolean Expression simplification: (Using Boolean Algebraic Manipulation)

\* Simplify:  $(\underline{x'y'z}) + (\underline{x'yz}) + (\underline{xy'})$

$$= \underline{x'z} (\underline{y+y'}) + xy'$$

$$= x'z \cdot 1 + xy'$$

$$= x'z + xy'$$

\* Simplify:

$$\underline{xy} + \underline{xy'}$$

$$= x(\underline{y+y'}) = x \cdot 1 = x$$

\* Simplify:

$$\underline{BC} + AB' + AB + \underline{BCD}$$

$$= \underline{BC} (\underline{1+D}) + AB' + AB$$

$$= BC \cdot 1 + \underline{AB'} + \underline{AB}$$

$$= BC + A(\underline{B'+B})$$

$$= BC + A \cdot 1$$

$$= BC + A$$



Prove,  $(A \oplus B)' = A \odot B$  using Boolean Manipulation:

$$\begin{aligned} & (A \oplus B)' \\ &= (AB' + A'B)' \\ &= (AB')' \cdot (A'B)' \quad \rightarrow \text{Applied DeMorgan} \\ &= (A' + B'') \cdot (A'' + B') \quad \rightarrow \text{" " " "} \\ &= (A' + B) \cdot (A + B') \quad \rightarrow \\ &= \underbrace{AA'} + A'B' + BA + \underbrace{BB'} \\ &= A'B' + BA \\ &= AB + A'B' \\ &= A \odot B \end{aligned}$$

Practice more & more.

Complement of a function:

if  $F = (x+y)$ , then its complement is  $F' = (x+y)'$

However, we can also find complement of a function by

1. Taking Dual of the function
2. Complement each variables

Example:

$$F = x'y z' + x' y' z$$

1. Dual =  $(x' + y + z') \cdot (x' + y' + z)$

2. Complement each var =  $(x + y' + z) \cdot (x + y + z') = F$

\* Find complement of  $x(y'z' + yz)$

$$1. \text{ Dual} = x + ((y' + z') \cdot (y + z))$$

$$2. \text{ Complement} = x' + (y + z) \cdot (y' + z')$$


$$\therefore F' = x' + (y + z)(y' + z')$$

# Using NAND or NOR to Draw circuit of a function:

## Steps:

 1. Represent the expression using AND, OR, NOT gate.
2. Draw each gate with equivalent NAND/NOR representation.
3. Remove any 2 cascading inverter.
4. Remove inverter from single input connection and replace input with its complement. (Only if there is a constraint)


Implement  $F = A(B + CD) + BC'$  using NAND only.



Now, if we want to reduce number of gates, we can remove cascading inverters.

$$\cancel{x} \text{ --- } \cancel{x'} \text{ --- } \cancel{x} = x \text{ ---}$$

A B C D

 

Therefore

A B C D

