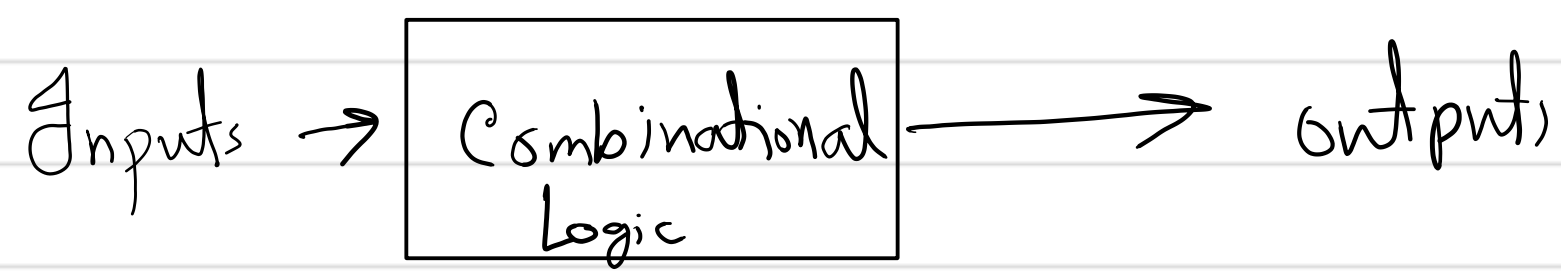



## Lecture Note 9

### Sequential Circuit

#### Combinational Circuits:



#### Sequential Circuits:

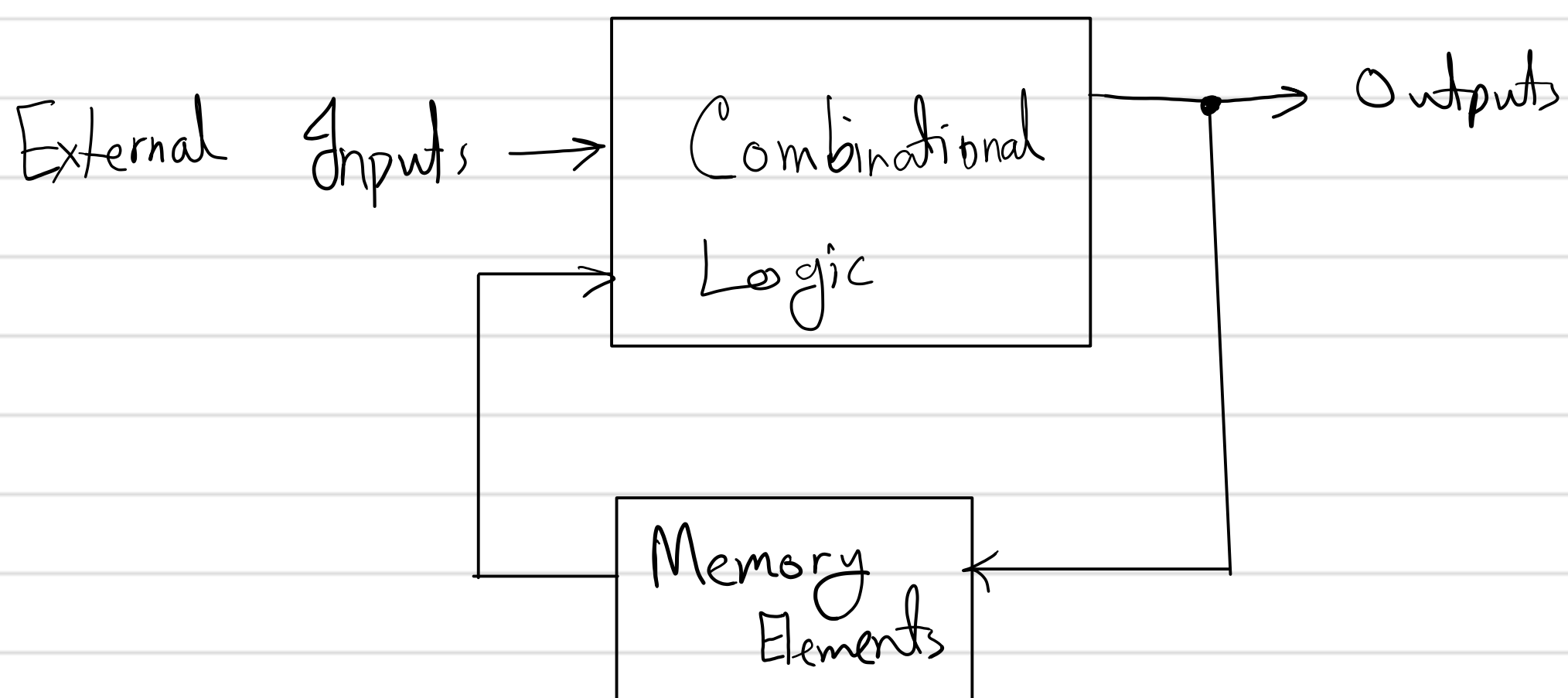

$$\text{Output}_t [Y(t+1)] = \text{External Inputs} + \text{Present state } [Y(t)]$$

#### Sequential circuits:



2 types: Synchronous: Output changes only at specific time.  
(Clock pulse)

Asynchronous: Output changes at any time. (Whenever we change inputs, doesn't depend on clock pulse.)

## Multivibrator:

A type of sequential circuit with different stability properties.

1. Astable: No stable state. Continuously switches.

Example: Clock pulse generator

2. Monostable: (1 stable state, another is temporary.)

Ex: When we punch our id card at

Baru, the gate opens. After a while the gate automatically closes.

If gate open = 1, and close = 0

then stable state is 0 (close)  
temporary " " 1 (open)

\* ② Bistable: 2 stable states (0,1).

Ex: Flipflop

## Memory Elements:

→ A device that can remember value indefinitely or change values in command.



$Q(t)$  = present state / current state /  $Q$

$Q(t+1)$  = next state - /  $Q^+$

To understand flipflop, we need to start from Latch.

# SR Latch (using NAND gate):


←  $Q(t)$

←  $\bar{Q}(t)$

## Deriving Truthtable:

### Case 1:

We don't need to know as one input is 0

 


$$S = 0 \quad R = 1 \quad Q = 1 \quad \bar{Q} = 0$$

NAND

X	Y	X NAND Y
0	0	1
0	1	1
1	0	0
1	1	0

∴ output 1 if any input = 0.


next iteration,

 

$$S = 1 \quad R = 1 \quad Q = 1 \quad \bar{Q} = 0$$


### Case 2:

We don't need to know as one input is 0

 


$$S = 1 \quad R = 0 \quad Q = 0 \quad \bar{Q} = 1$$

next iteration,

 

$$S = 1 \quad R = 1 \quad Q = 0 \quad \bar{Q} = 1$$

### Case 3:

 

$$S = 0$$

$$R = 0$$

$$Q = 1$$

$$\overline{Q} = 1$$

$Q$  &  $\overline{Q}$  can't be one at the same time.  
 $\therefore$  Invalid / Not used

$\therefore$  Truth table:

S	R	Q	$\overline{Q}$
0	0	Invalid / Not used	
0	1	1	0
1	0	0	1
1	1	memory	

Difference Between SR Latch & flipflop:

\* Latch: Input can be changed at any time

\* Flipflop: Input can be changed only when clk = 1 or high.

### Flipflops

We will learn about SR, D, JK & T flipflops.

We need to know their,


→ Circuit & Block Diagram

→ Truth table (Inputs | outputs)

→ Characteristic table (Present state + Input | next state)

→ Excitation table (Present state + Next state | inputs)

## SR Flipflop

 

$$S^* = (S \cdot \text{clk})' = S' + \text{clk}' = S' + 1' = S' + 0 = S'$$

$$R^* = (R \cdot \text{clk})' = R' + \text{clk}' = R' + 1' = R' + 0 = R'$$

Since, FF only work when  $\text{clk} = 1$

## Truth table:

S	R	$S^*$	$R^*$	Q	$\bar{Q}$
0	0	1	1	memory/no change	
0	1	1	0	0	1
1	0	0	1	1	0
1	1	0	0	not used	

This is written only to understand. In exams, you can skip  $S^*$  &  $R^*$

## Characteristic Table: (Depending on flipflops inputs & present state, what would be the next state?)

Present state $Q(t)$	inputs S R		next state $Q(t)+1$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	not used
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	not used

## Excitation Table:

\* Analyzing the flipflop present & next state, we try to determine the inputs. (we fill the input column by analysing characteristic table.)

Present state		next state		inputs		Q(t)	S	R	Q(t)+1
Q(t)	Q(t+1)			S	R				
0	0			0	X	0	0	0	0
0	1			1	0	0	1	0	1
1	0			0	1	1	0	0	0
1	1			X	0	1	1	0	1


(Note: In the original image, the next state 1 is marked as "not used" for Q(t)=0 and Q(t)=1. The inputs S and R are also marked with "not used" for certain combinations.)

∴ Excitation table

Q(t)	Q(t+1)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

If we have different value for S or R in different rows, then we write X, Don't care


Block Diagram:

 


 
# D Flipflops

→ Motivation: SR has invalid input which can be removed.



# we merged S & R using NOT Gate and call it D.

Then,  $D = S$   
 $D = R = S'$

Truth table:

D	Q	$\overline{Q}$
0	0	1
1	1	0

Characteristic Table:

Q(t)	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

# next state doesn't depend on Q(t)/present state.


∴ It doesn't have memory state.

Excitation Table:


Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

# Present state doesn't matter

Block Diagram:

 

using SR,

 


## JK Flipflop:

Motivation: SR FF has invalid state/unused input (11)

D FF has no present state/memory

JK Flipflop has a new output, Toggle.

 next state = previous state  
 $Q(t+1) = [Q(t)]'$



## Truth table:

J	K	Q	$\bar{Q}$
0	0	Memory	
0	1	0	1
1	0	1	0
1	1	Toggle	


## Characteristic Table:

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

## Excitation table:

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

## Block Diagram:

 




## T flipflop:

\* If we short  $\bar{J}$  &  $K$  in  $\bar{J}K$  Flipflop, we get T flipflop

$$\bar{J} = T$$

$$K = T$$

 

## Truth table:

T	Q	$\bar{Q}$
0	No change	
1	Toggle	

## Characteristic Table:

$Q(t)$	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

## Excitation table:

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

## Block Diagram:



using  $\bar{J}K$ ,

